



Wiring Tangle...

Only one of these four switches has power and will turn the light bulb on when flipped. What is the color of the switch you should pick to do the job?